

Simulation Exercise 5.5  
4-Bit Adder/Subtractor with Seven Segment  
Display  
ELEE 2640

Benyamain YACOOB

March 2, 2024

Date Performed:	March 5, 2024
Partners:	Ara OLADIPO Andre PRICE
Instructor:	Professor PAULIK



## Contents

<b>1 Objectives</b>	<b>4</b>
<b>2 Problem Statement</b>	<b>4</b>
<b>3 Materials</b>	<b>4</b>
<b>4 Requirements</b>	<b>4</b>
<b>5 Seven Segment Display Decoder</b>	<b>9</b>
5.1 Seven Segment Display Decoder Truth Table . . . . .	9
5.2 Seven Segment Display Decoder Implementation Code . . . . .	9
5.3 Seven Segment Display Elaborated Design Schematic . . . . .	10
5.4 Seven Segment Display Decoder Elaborated Design Schematic . . .	10
5.5 Seven Segment Synthesized Design . . . . .	11
5.6 Seven Segments Synthesized Schematic . . . . .	11
5.7 Seven Segment Display Test Bench . . . . .	12
5.7.1 Seven Segment Display Decoder Test Bench Implementation Code . . . . .	12
5.7.2 Seven Segment Display Decoder Test Bench Behavioral Sim- ulation . . . . .	13
5.7.3 Seven Segment Display Decoder Test Bench Schematic . . .	14
5.7.4 Seven Segment Display Decoder Post Synthesis Timing Sim- ulation . . . . .	15
5.7.5 Seven Segment Display Decoder Constraints File . . . . .	16
5.7.6 Seven Segment Display Decoder Console Output . . . . .	16
5.8 Results and Analysis Discussion . . . . .	16
<b>6 4-Bit Adder/Subtractor with Seven Segment Display Decoder</b>	<b>18</b>
6.1 4-Bit Adder/Subtractor with Seven Segment Display Decoder Imple- mentation Code . . . . .	18
6.2 4-Bit Adder/Subtractor with Seven Segment Display Decoder RTL Schematic . . . . .	19
6.3 4-Bit Adder/Subtractor with Seven Segment Display Decoder Syn- thesized Design . . . . .	19
6.4 4-Bit Adder/Subtractor with Seven Segment Display Decoder Test Bench . . . . .	20
6.4.1 4-Bit Adder/Subtractor with Seven Segment Display Decoder Test Bench Code . . . . .	20
6.4.2 4-Bit Adder/Subtractor with Seven Segment Display Decoder Test Bench Behavioral Simulation . . . . .	21
6.4.3 4-Bit Adder/Subtractor with Seven Segment Display Decoder Test Bench Console Output . . . . .	21
6.4.4 4-Bit Adder/Subtractor with Seven Segment Display Decoder Test Bench Post Synthesis Timing Simulation . . . . .	22
6.5 Results and Analysis Discussion . . . . .	22

<b>7</b>	<b>Project Summary</b>	<b>23</b>
<b>8</b>	<b>Results and Conclusion</b>	<b>23</b>
<b>9</b>	<b>Group Contributions</b>	<b>24</b>

# 1 Objectives

## First Objective

Code in SystemVerilog for combinational logic design and testing.

## Second Objective

Simulate and implement combinational circuits using Xilinx Vivado integrated development environment (IDE).

## Third Objective

Complete adder/subtractor work with a seven segment result display.

# 2 Problem Statement

In this simulation exercise, you will follow the work you did in Simulation Exercise #5 by adding a Seven Segment display subsystem similar to that developed in Simulation Exercise #3, but modified to display the full range of hexadecimal digits. You will be using the SystemVerilog hardware description language (HDL) and the Xilinx ISE(introduced in Simulation Exercise #4) to implement your designs.

# 3 Materials

Xilinx integrated synthesis environment (ISE)

# 4 Requirements

## Schematic

 


Figure 1: RTL Schematic for 4-Bit Adder/Subtractor

 


Figure 2: Top-Level Schematic for 4-Bit Adder with Decoder

### Seven Segment Display Format

 


Figure 3: Seven Segment Display Segments and Diodes

### HEX Data Display on Seven Segment Device Format



Figure 4: HEX Data Display on Seven Segment Device

#### IO Devices

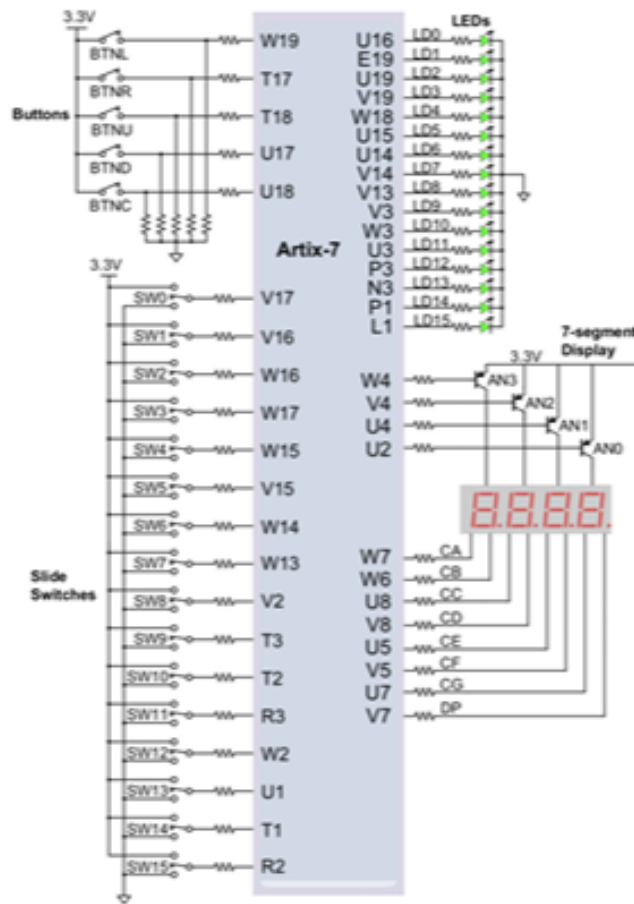


Figure 16. General Purpose I/O devices on the Basys3

Figure 5: General Purpose IO Devices on the Basys3

Truth Table

S4	S3	S2	S1	Hex	a	b	c	d	e	f	g
0	0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	1							
0	0	1	0	2							
0	0	1	1	3							
0	1	0	0	4							
0	1	0	1	5							
0	1	1	0	6							
0	1	1	1	7							
1	0	0	0	8							
1	0	0	1	9							
1	0	1	0	A							
1	0	1	1	B							
1	1	0	0	C							
1	1	0	1	D							
1	1	1	0	E							
1	1	1	1	F							

Figure 6: Truth Table for Seven Segment Display Decoder



## 5 Seven Segment Display Decoder

### 5.1 Seven Segment Display Decoder Truth Table

S4	S3	S2	S1	Hex	a	b	c	d	e	f	g
0	0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	1	1	0	0	1	1	1	1
0	0	1	1	2	0	0	1	0	0	1	0
0	1	0	0	3	0	0	0	0	1	1	0
0	1	0	1	4	1	0	0	1	1	0	0
0	1	1	0	5	0	1	0	0	1	0	0
0	1	1	1	6	0	1	0	0	0	0	0
1	0	0	0	7	0	0	0	1	1	1	1
1	0	0	0	8	0	0	0	0	0	0	0
1	0	0	1	9	0	0	0	0	1	0	0
1	0	1	0	A	0	0	0	1	0	0	0
1	0	1	1	B	1	1	0	0	0	0	0
1	1	0	0	C	0	1	1	0	0	0	1
1	1	0	1	D	1	0	0	0	0	1	0
1	1	1	0	E	0	1	1	0	0	0	0
1	1	1	1	F	0	1	1	1	0	0	0

Figure 7: Truth Table for Seven Segment Display Decoder

### 5.2 Seven Segment Display Decoder Implementation Code

```

1  timescale 1ns / 1ps
2  //////////////////////////////////////
3  // Company: University of Detroit Mercy
4  // Engineer: Benyamin Yacoub, Andre Price, Eyiara Oladipo
5  //
6  // Create Date: 03/09/2024 4:30:00 PM
7  // Design Name: sevenseg
8  // Module Name: sevenseg
9  // Project Name: Simulation_Assignment_5.5
10 // Target Devices:
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 //////////////////////////////////////
21
22
23 module sevenseg(
24     input logic [3:0] data,
25     output logic [6:0] segments,
26     output logic [3:0] Anode_Activate
27 );
28     always_comb
29     case (data)
30         // common anode inverted encoding is necessary

```

Figure 8: Seven Segment Display Decoder Implementation Code

### 5.3 Seven Segment Display Elaborated Design Schematic

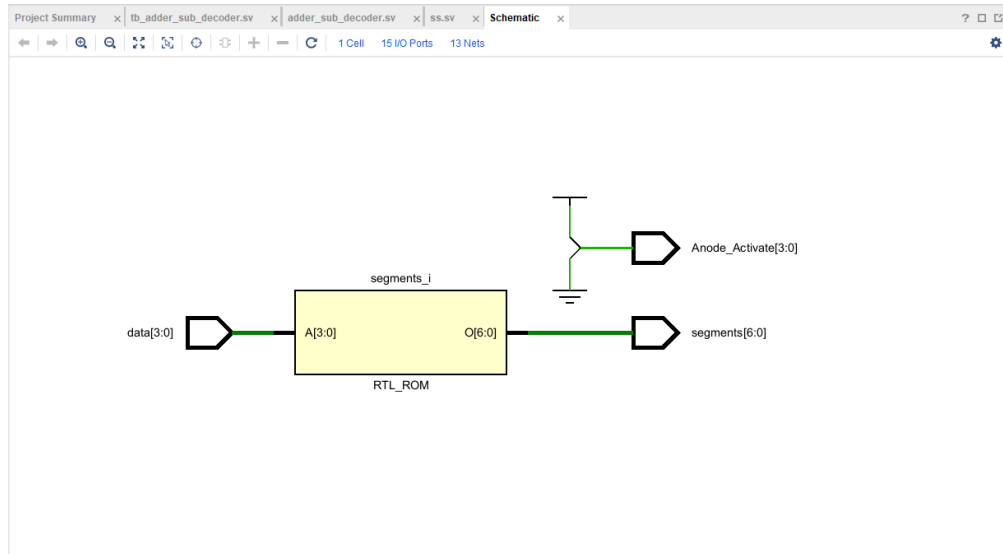


Figure 9: Seven Segment Display Elaborated Design Schematic

### 5.4 Seven Segment Display Decoder Elaborated Design Schematic

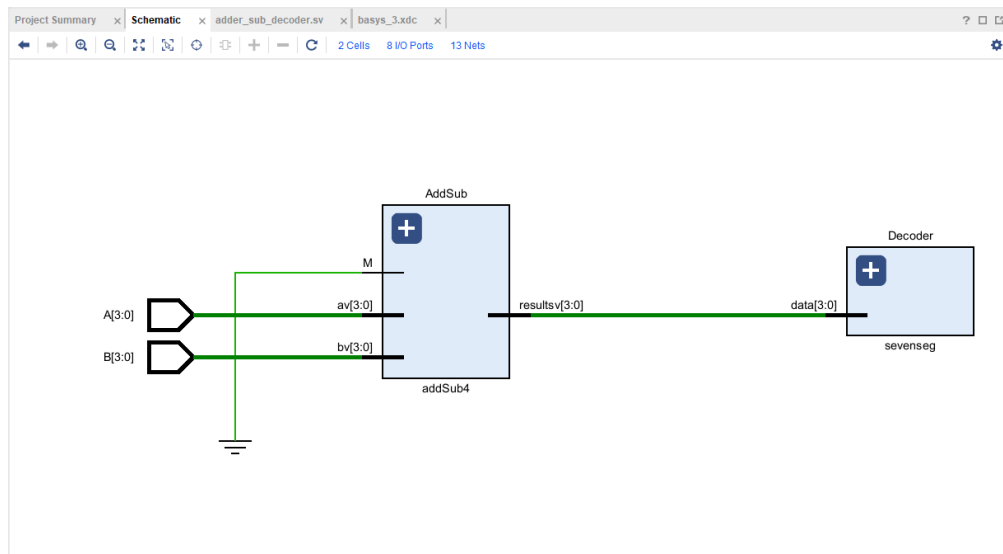


Figure 10: Seven Segment Display Decoder Elaborated Design Schematic

## 5.5 Seven Segment Synthesized Design

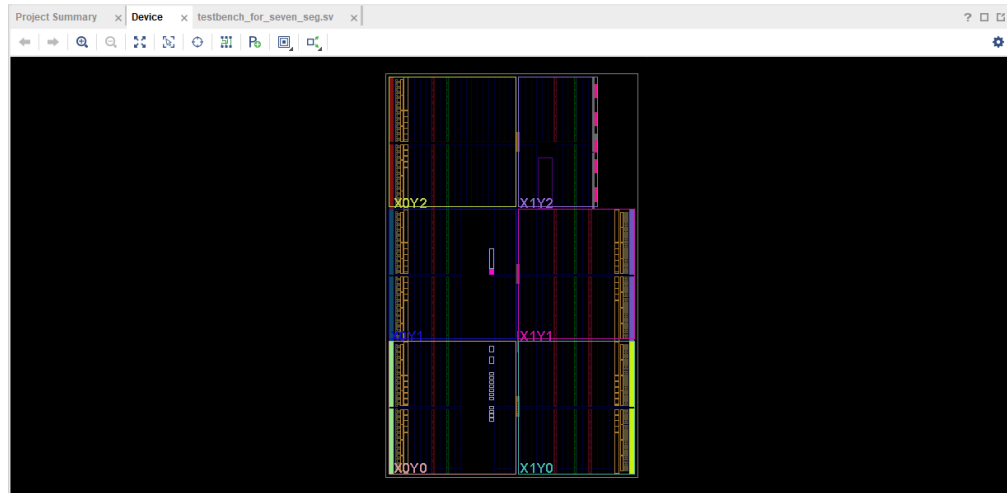


Figure 11: Seven Segment Display Decoder Synthesized Design

## 5.6 Seven Segments Synthesized Schematic


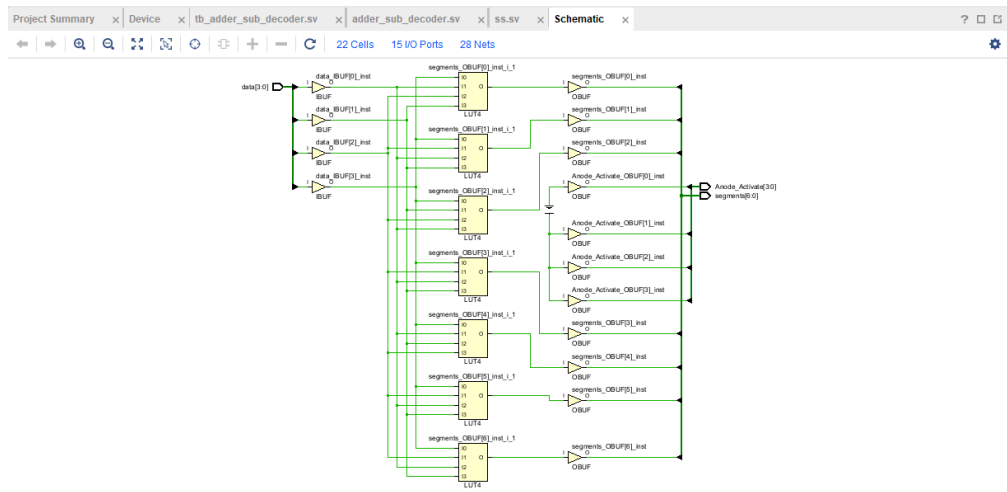


Figure 12: Seven Segment Display Decoder Synthesized Schematic

## 5.7 Seven Segment Display Test Bench
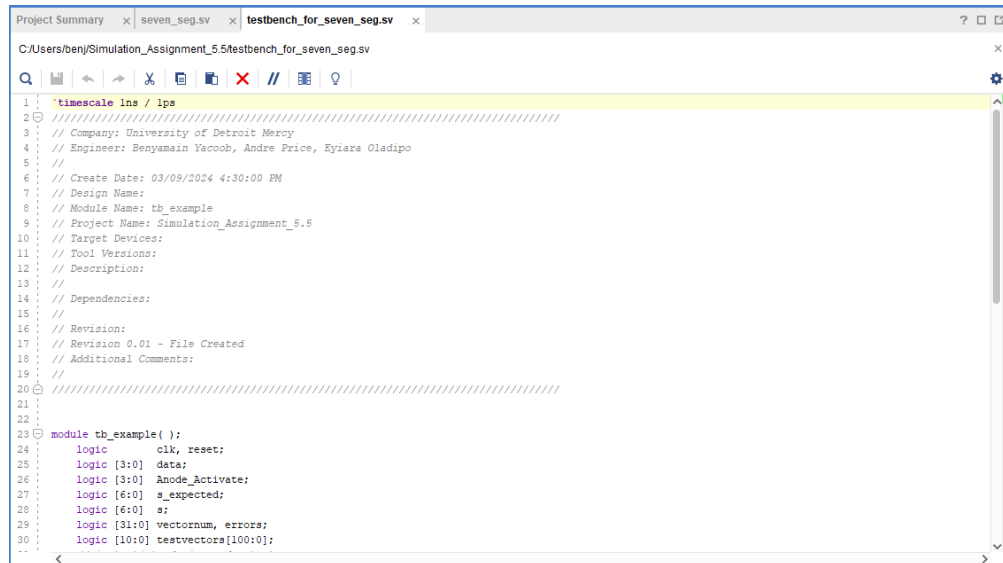
### 5.7.1 Seven Segment Display Decoder Test Bench Implementation Code



```
1 timescale 1ns / 1ps
2 //////////////////////////////////////////////////
3 // Company: University of Detroit Mercy
4 // Engineer: Benyamain Yacoub, Andre Price, Eyiara Gladipo
5 //
6 // Create Date: 03/09/2024 4:30:00 PM
7 // Design Name:
8 // Module Name: tb_example
9 // Project Name: Simulation_Assignment_5.5
10 // Target Devices:
11 // Tool Versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 //////////////////////////////////////////////////
21
22
23 module tb_example( );
24     logic    clk, reset;
25     logic [3:0] data;
26     logic [3:0] Anode_Activate;
27     logic [6:0] s_expected;
28     logic [6:0] s;
29     logic [31:0] vectornum, errors;
30     logic [10:0] testvectors[100:0];
31
```

Figure 13: Test Bench Implementation Code

### 5.7.2 Seven Segment Display Decoder Test Bench Behavioral Simulation

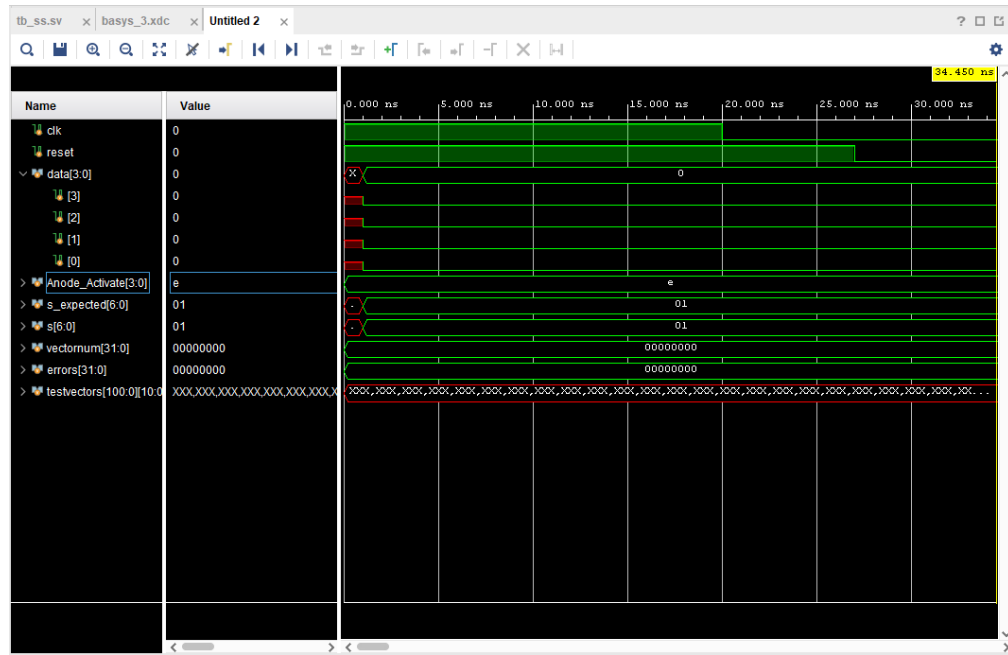


Figure 14: Test Bench Behavioral Simulation

### 5.7.3 Seven Segment Display Decoder Test Bench Schematic

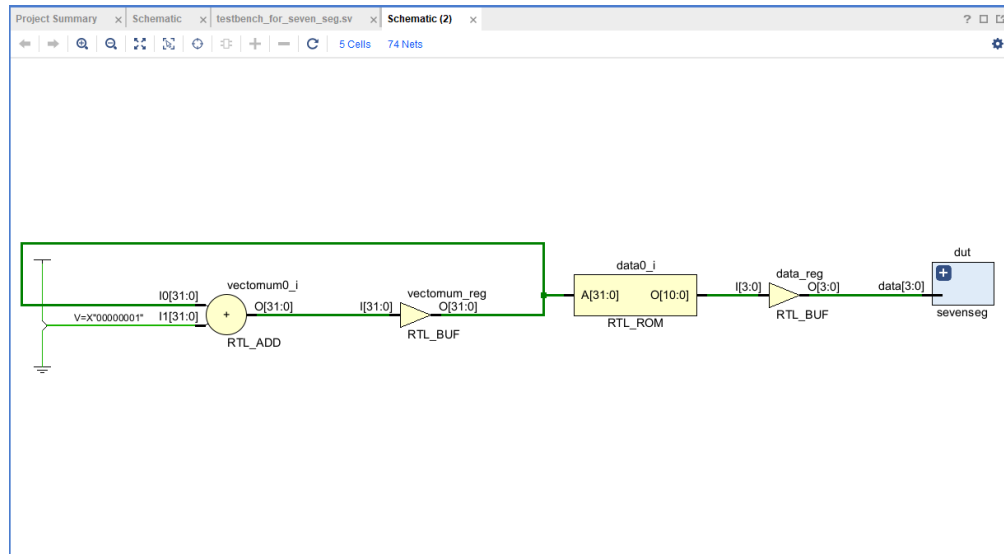


Figure 15: Test Bench Schematic

### 5.7.4 Seven Segment Display Decoder Post Synthesis Timing Simulation


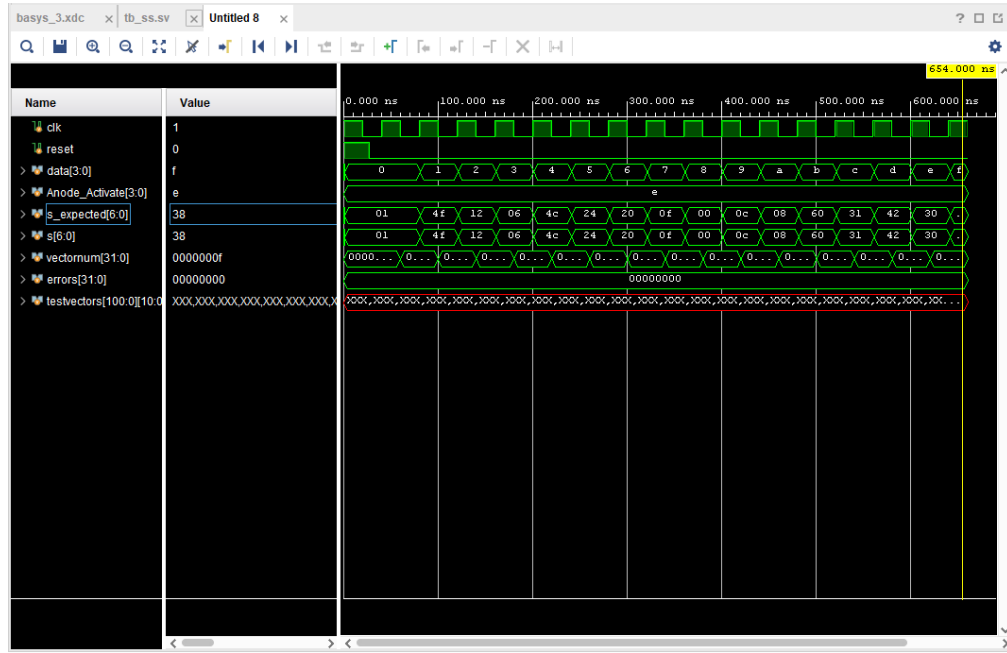


Figure 16: Test Bench Post Synthesis Timing Simulation
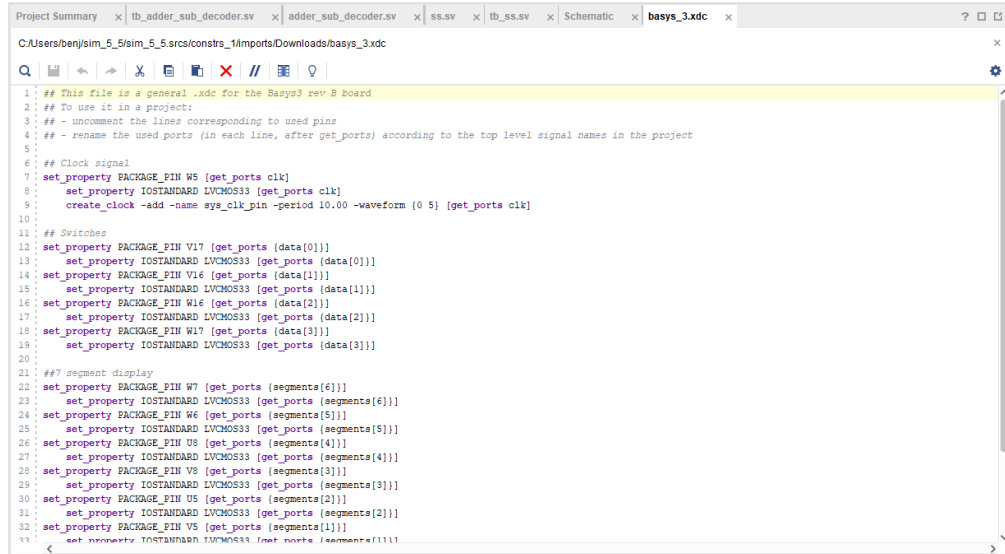
### 5.7.5 Seven Segment Display Decoder Constraints File



```
1 ## This file is a general .xdc for the Basys3 rev B board
2 ## To use it in a project:
3 ## - uncomment the lines corresponding to used pins
4 ## - rename the used ports (in each line, after get_ports) according to the top level signal names in the project
5
6 ## Clock signal
7 set_property PACKAGE_PIN W5 [get_ports clk]
8 set_property IOSTANDARD LVCMOS33 [get_ports clk]
9 create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports clk]
10
11 ## Switches
12 set_property PACKAGE_PIN V17 [get_ports {data[0]}]
13 set_property IOSTANDARD LVCMOS33 [get_ports {data[0]}]
14 set_property PACKAGE_PIN V16 [get_ports {data[1]}]
15 set_property IOSTANDARD LVCMOS33 [get_ports {data[1]}]
16 set_property PACKAGE_PIN W16 [get_ports {data[2]}]
17 set_property IOSTANDARD LVCMOS33 [get_ports {data[2]}]
18 set_property PACKAGE_PIN W17 [get_ports {data[3]}]
19 set_property IOSTANDARD LVCMOS33 [get_ports {data[3]}]
20
21 ##7 segment display
22 set_property PACKAGE_PIN W7 [get_ports {segments[6]}]
23 set_property IOSTANDARD LVCMOS33 [get_ports {segments[6]}]
24 set_property PACKAGE_PIN W6 [get_ports {segments[5]}]
25 set_property IOSTANDARD LVCMOS33 [get_ports {segments[5]}]
26 set_property PACKAGE_PIN U8 [get_ports {segments[4]}]
27 set_property IOSTANDARD LVCMOS33 [get_ports {segments[4]}]
28 set_property PACKAGE_PIN V8 [get_ports {segments[3]}]
29 set_property IOSTANDARD LVCMOS33 [get_ports {segments[3]}]
30 set_property PACKAGE_PIN U5 [get_ports {segments[2]}]
31 set_property IOSTANDARD LVCMOS33 [get_ports {segments[2]}]
32 set_property PACKAGE_PIN V5 [get_ports {segments[1]}]
33 set_property IOSTANDARD LVCMOS33 [get_ports {segments[1]}]
```

Figure 17: Basys3 Constraints File

### 5.7.6 Seven Segment Display Decoder Console Output

```
# KERNEL: SLP SIMULATION INITIALIZATION DONE - TIME: 0.0 [s].
# KERNEL: Kernel process initialization done.
# Allocation: Simulator allocated 4670 kB (elbread=427 elab2=4109 kernel=134 sdf=0)
# KERNEL: ASDB file was created in location /home/runner/dataset.asdb
# KERNEL: 16 tests completed with 0 errors
# RUNTIME: Info: RUNTIME 0068 testbench.sv (63): $finish called.
```

Figure 18: Seven Segment Display Decoder Console Output

## 5.8 Results and Analysis Discussion

*Provide a detailed explanation of the RTL schematic hardware generated and associate each element with the corresponding code. Essentially, you need to explain the code-to-hardware relationship?*

The schematic diagram shows two inputs, *A* and *B*, correlating with the adder-subtractor inputs in the code. The *M* input determines whether the adder-subtractor acts as a subtractor or as an adder. The adder-subtractor's output is fed into the seven segment decoder (*sevenseg* module), which generates an output mirroring the results from the earlier truth table.

*What is the delay from an input change to a stable digit input and segment output value when performing a post synthesis timing simulation?*




The delay from an input change to a stable *digit* input and *segment* output value when performing a post synthesis timing simulation is about 20 nanoseconds (*ns*). We find this value by measuring the endpoint of when an active high of a stable digital input is simulated, after which we find the time gap from the endpoint of stable input to the start of segment output value. Therefore, the difference in delay can be modeled from the equation below, but the final result should be 20 *ns*. We define active as when the simulation showcases the state of either being active low signal or high signal. To account for the differences in readings, we should mention that we do not expect the delay that we recorded to be exact with what is measured in the rubric.

$$Delay = Segment_{OUT} - Digit_{IN} \quad (1)$$

This section paved the way to showing the group specifically how the rest of the simulation assignment was going to go. That conclusion being filled with galling issues and warnings. The group spent a lot of time trying to debug Vivado, some methods being renaming some files, checking environment variables to ensure that everything was accurate, or even restarting the entire software. It seemed as if no matter what we did, we kept getting the "***spawn failed, no error***" message. At times, our schematic files didn't even open, which made taking screenshots or verifying our work much difficult than previously. With so many issues regarding bugs, this section, and this simulation assignment in general, proved itself to be much more insufferable than any of the other previous one, no matter their difficulty.

## 6 4-Bit Adder/Subtractor with Seven Segment Display Decoder
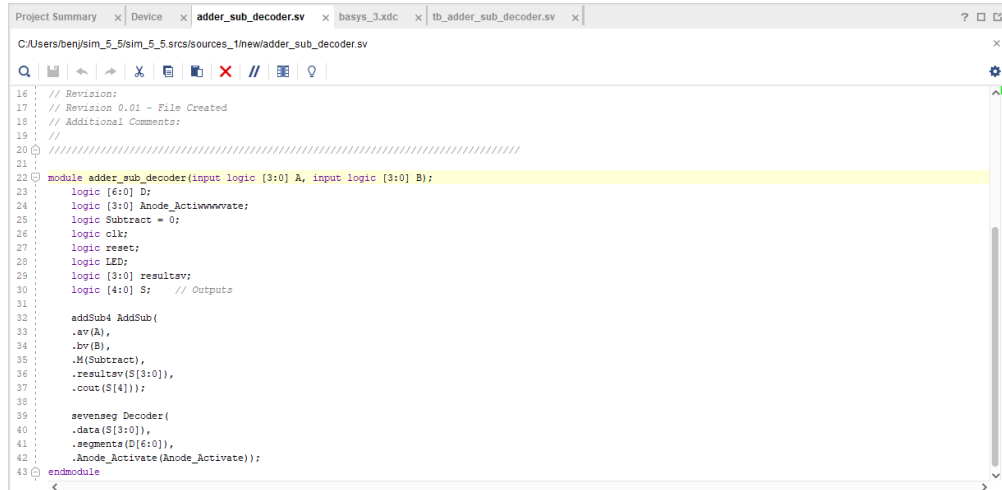
### 6.1 4-Bit Adder/Subtractor with Seven Segment Display Decoder Implementation Code



```
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////////////////////
21
22 module adder_sub_decoder(input logic [3:0] A, input logic [3:0] B);
23     logic [6:0] D;
24     logic [3:0] Anode_Activate;
25     logic Subtract = 0;
26     logic clk;
27     logic reset;
28     logic LED;
29     logic [3:0] resultsv;
30     logic [4:0] S; // Outputs
31
32     addSub4 AddSub(
33         .av(A),
34         .bv(B),
35         .H(Subtract),
36         .resultsv(S[3:0]),
37         .cout(S[4]));
38
39     sevenseg Decoder(
40         .data(S[3:0]),
41         .segments[D[6:0]],
42         .Anode_Activate(Anode_Activate));
43 endmodule
```

Figure 19: 4-Bit Adder/Subtractor with Seven Segment Display Decoder Implementation Code

## 6.2 4-Bit Adder/Subtractor with Seven Segment Display Decoder RTL Schematic

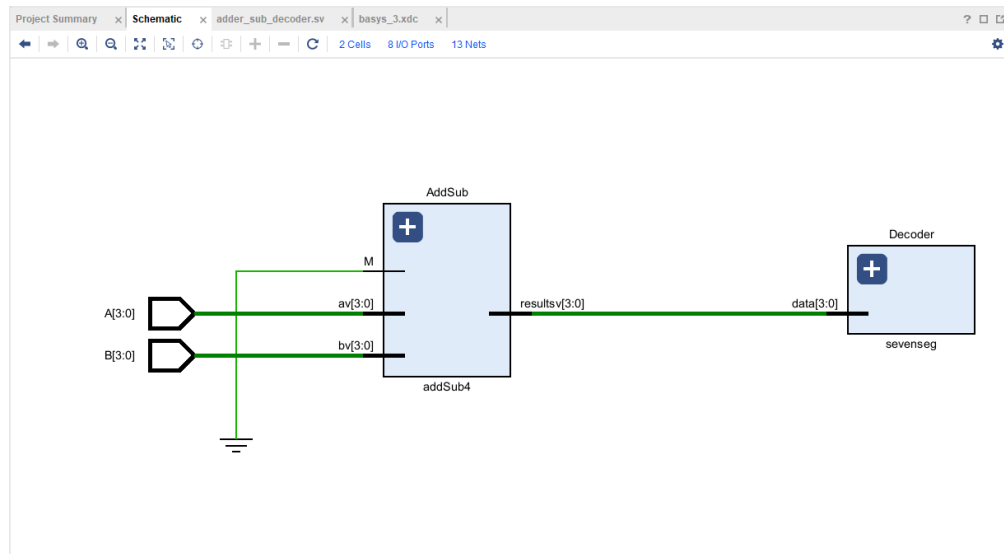


Figure 20: RTL Schematic

## 6.3 4-Bit Adder/Subtractor with Seven Segment Display Decoder Synthesized Design

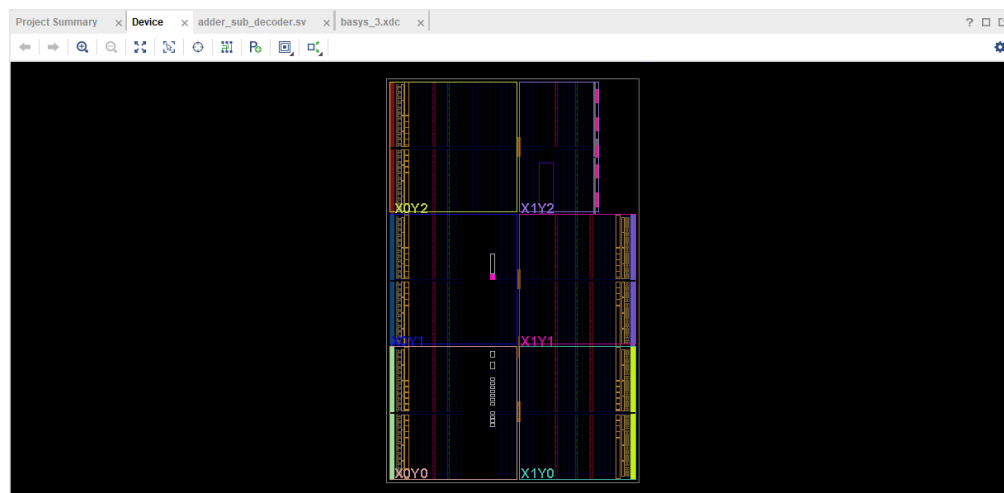


Figure 21: Synthesized Design

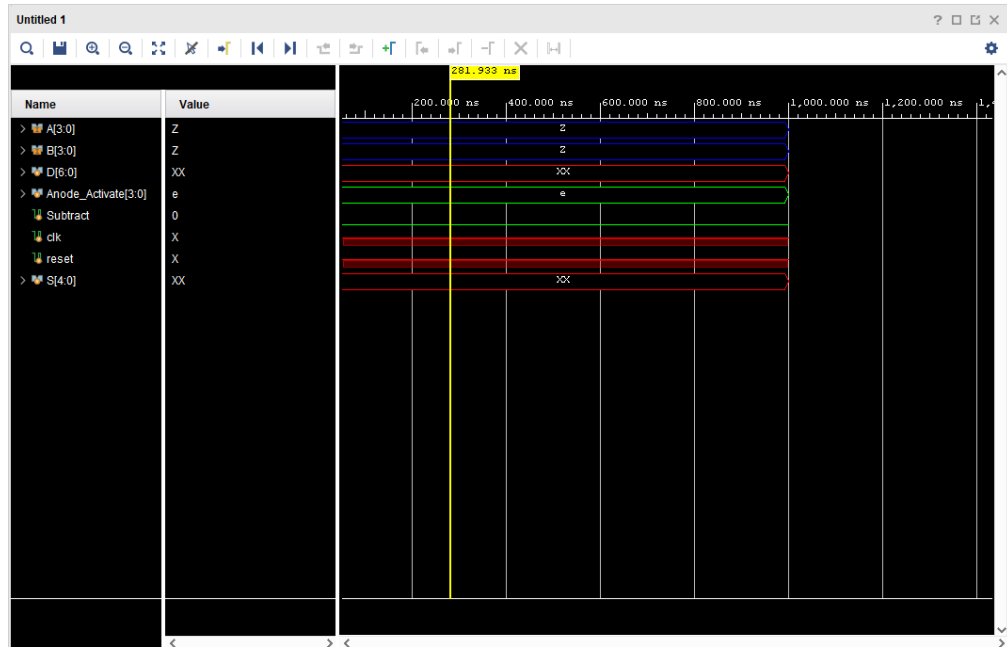


Figure 22: Behavioral Simulation

## 6.4 4-Bit Adder/Subtractor with Seven Segment Display Decoder Test Bench

### 6.4.1 4-Bit Adder/Subtractor with Seven Segment Display Decoder Test Bench Code

```

Project Summary | Device | adder_sub_decoder.v | basys_3.xdc | tb_adder_sub_decoder.v |
C:/Users/ben/sim_5/sim_5_5/srcs/sim_3new/tb_adder_sub_decoder.v

16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////////////////////
21
22
23 module tb_adder_sub_decoder();
24     logic [3:0] a; logic [3:0] b; logic Subtract;
25
26     // Outputs
27     logic [3:0] result; logic carry;
28
29     logic clk, reset; integer i;
30
31     addSub4 DUT(
32         .av(a),
33         .bv(b),
34         .M(Subtract),
35         .resultv(result),
36         .cout(carry)
37     );
38
39     adder_sub_decoder asd(
40         .A(a),
41         .B(b)
42     );
43

```

Figure 23: Test Bench Code

#### 6.4.2 4-Bit Adder/Subtractor with Seven Segment Display Decoder Test Bench Behavioral Simulation

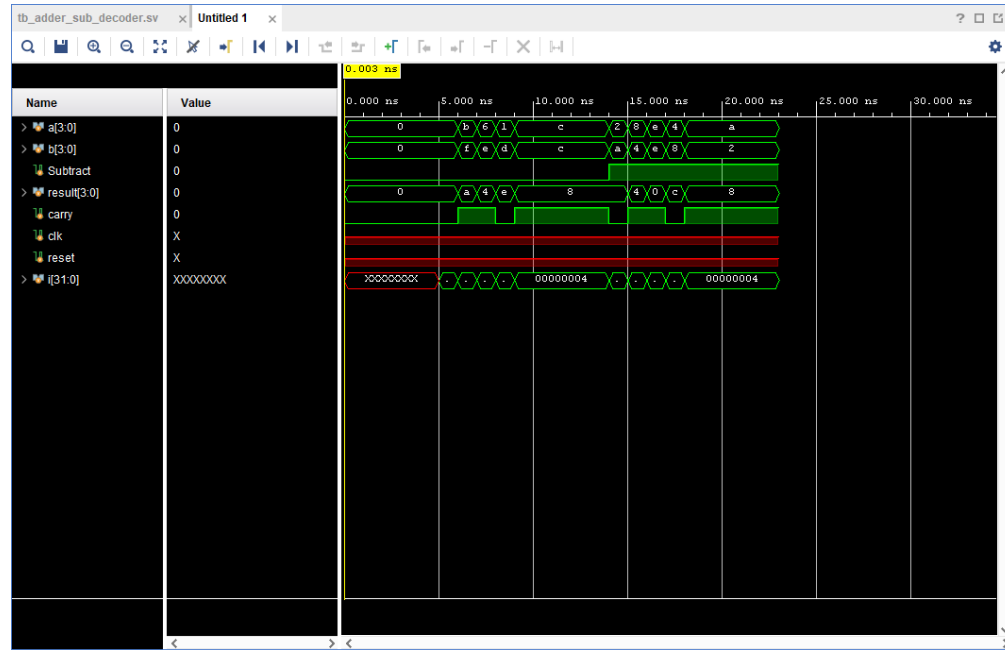


Figure 24: Test Bench Behavioral Simulation

#### 6.4.3 4-Bit Adder/Subtractor with Seven Segment Display Decoder Test Bench Console Output

```
# run 6000ns
At time 0.00 ns: a= 0, b= 0, Subtract=0, carry=0, Result=0, Segments=0
At time 6.00 ns: a=11, b=15, Subtract=0, carry=1, Result=a, Segments=f
At time 7.00 ns: a= 6, b=14, Subtract=0, carry=1, Result=4, Segments=e
At time 8.00 ns: a= 1, b=13, Subtract=0, carry=0, Result=e, Segments=d
At time 9.00 ns: a=12, b=12, Subtract=0, carry=1, Result=8, Segments=c
At time 14.00 ns: a= 2, b=10, Subtract=1, carry=0, Result=8, Segments=5
At time 15.00 ns: a= 8, b= 4, Subtract=1, carry=1, Result=4, Segments=b
At time 16.00 ns: a=14, b=14, Subtract=1, carry=1, Result=0, Segments=1
At time 17.00 ns: a= 4, b= 8, Subtract=1, carry=0, Result=c, Segments=7
At time 18.00 ns: a=10, b= 2, Subtract=1, carry=1, Result=8, Segments=d
```

Figure 25: Test Bench Behavioral Simulation Console Output

#### 6.4.4 4-Bit Adder/Subtractor with Seven Segment Display Decoder Test Bench Post Synthesis Timing Simulation

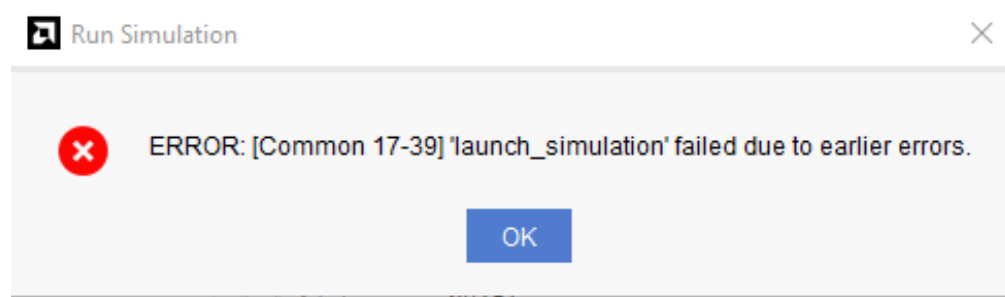


Figure 26: Test Bench Post Synthesis Timing Simulation Error #1

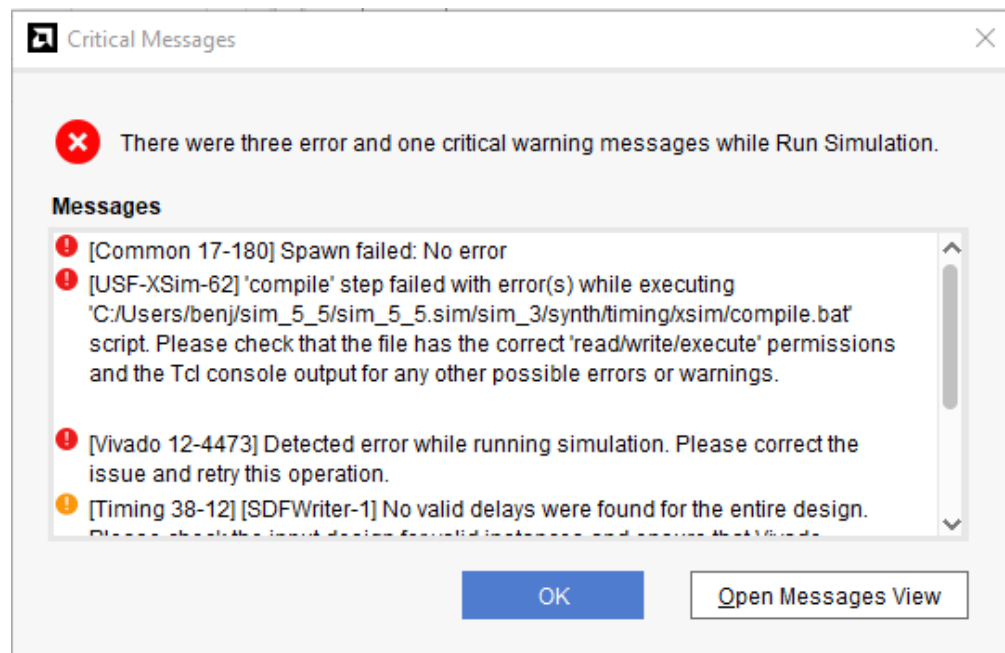


Figure 27: Test Bench Post Synthesis Timing Simulation Error #2

### 6.5 Results and Analysis Discussion

The 4-bit adder and subtractor section continued the trend of exasperation displayed in the first section, but somehow much worse. This section involved issues such as files not running because of extra spaces and difficulties coding the test benches. There were times when the technical difficulties were so abundant that the group almost gave up. *We were not able to open synthesized design schematic for seven*

*segment decoder adder subtractor post synthesis timing simulation for the test bench seven segment decoder adder subtractor was not completed.*

Despite the efforts made by the group, the errors highlighted in the previous paragraph still remain present due to difficulties coming up with solutions for them. The fact that those errors are there with no clear solution in mind highlights the difficulty present in the simulation assignment. The group hopes to ask questions pertaining to the solutions for these problems to the professor.

## 7 Project Summary

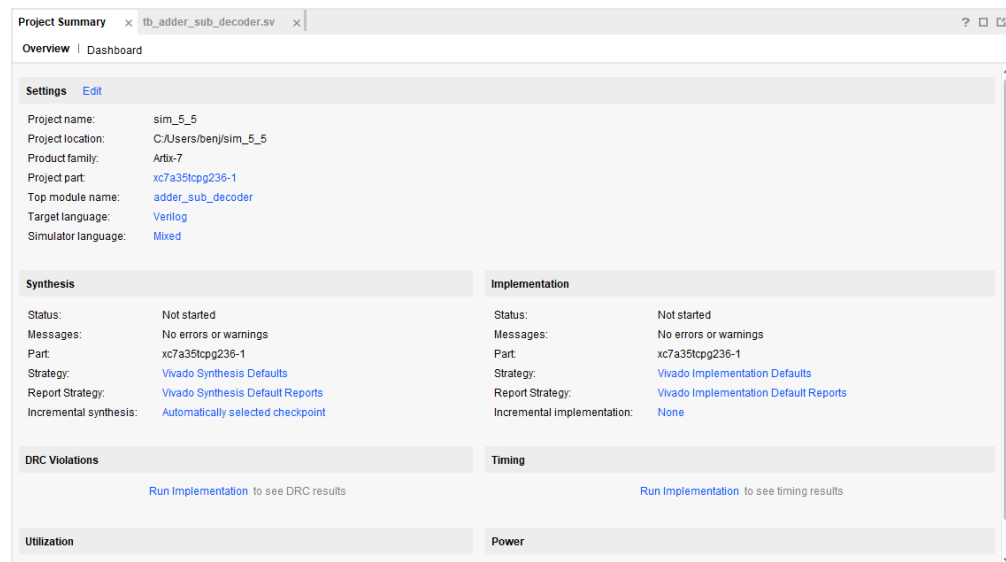


Figure 28: Project Summary

## 8 Results and Conclusion

This section discusses the results of the Vivado simulation experiments. The discussion provides in-depth explanations of the results and any discrepancies between the results and theoretical expectations. It also explores potential sources of error and discusses the accuracy of the tests, the debugging process, and what was learned from these experiences.

Simulation Exercise #5.5 was aided in large by the help of the original Simulation Exercise #5. This major aspect of the exercise provided a semblance of familiarity with the topic and allowed the group to remain on the same page when it comes to the understanding of the material presented. As per the trend for all previous

simulation exercises, this one also had its own share of complexity that forced the group to think.

However, there were some forms of complexity that went beyond the conceptual material needed for the simulation exercise. This was mainly in regards to the large amount of bugs and errors when coding both the seven segment displays and the 4-bit adder and subtractor. There were times when files refused to open because of spaces in the log files or when Vivado would run files different from the ones we wanted. This lowered group morale at large since some issues were based on the software itself breaking. With a lot of turning the software on and off and deleting spaces, we eventually were able to get the screenshot we needed for the report, despite doing so taking a long time to do.

## **9 Group Contributions**

The work for this simulation assignment was divided among three individuals: Benyamain Yacoob, Andre Price Jr, and Eyiara Oladipo. Andre and Benyamain collaborated using Vivado software and writing in SystemVerilog to code the circuits. It should be noted, however, that this was a group effort and all members were present to answer any questions related to the circuits. Benyamain and Eyiara took the lead with the formatting and organizing the Overleaf document. Benyamain proofread the document before submitting.